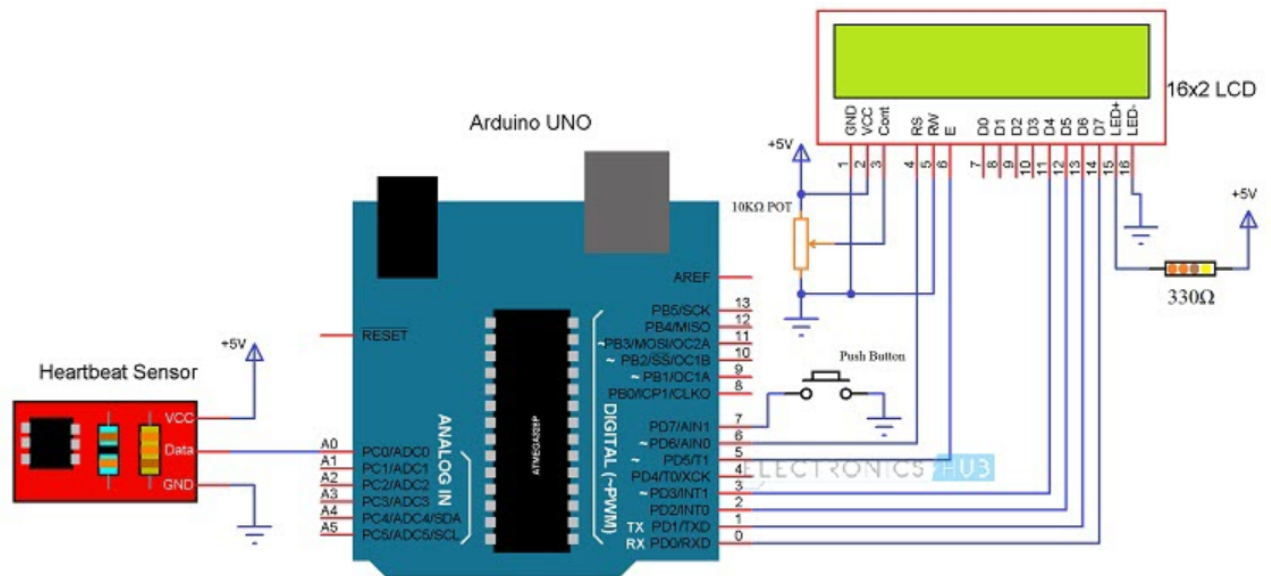


AE242
Group 9
Heart beat sensor project

Circuit diagram



Component required

Components Required

- Arduino UNO x 1
- 16 x 2 LCD Display x 1
- 10KΩ Potentiometer
- 330Ω Resistor (Optional – for LCD backlight)
- Push Button
- Heartbeat Sensor Module with Probe (finger-based)
- Mini Breadboard
- Connecting Wires